
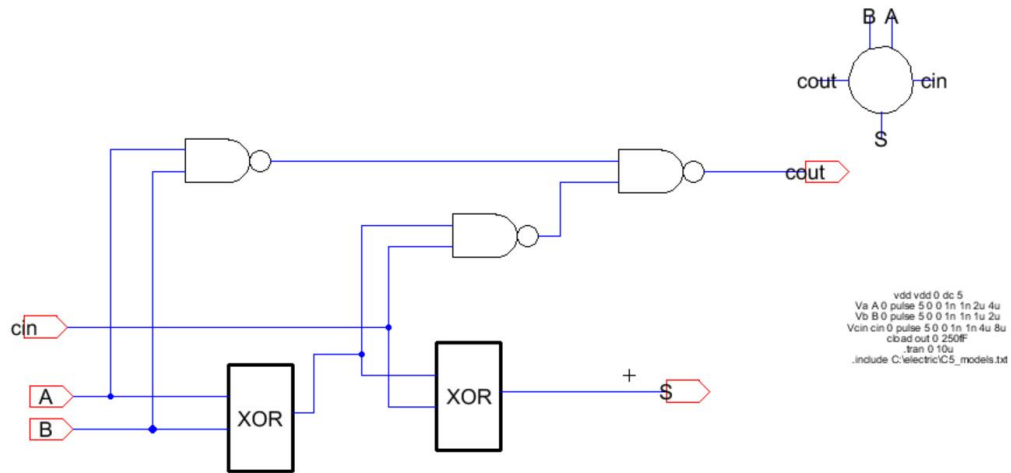


VLSI DESIGN in Electric Software


One bit Full-adder : Schematic

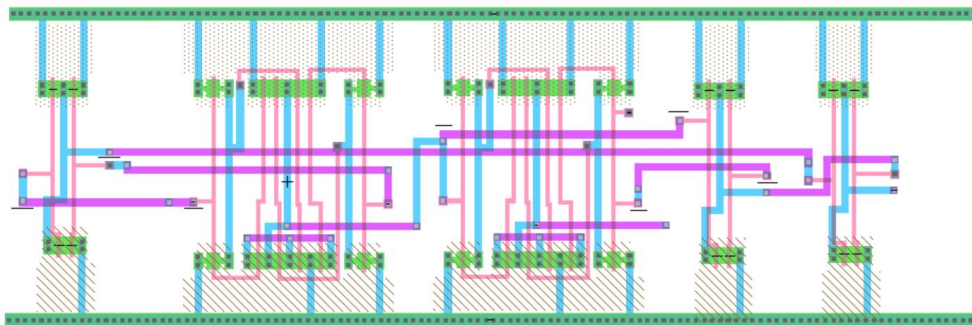


Layout:




No DRC, NCC errors:

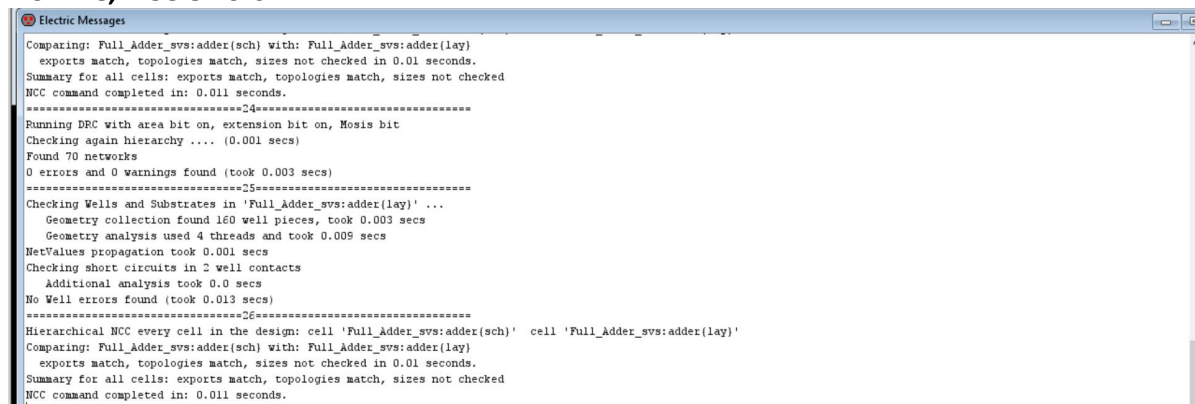

D-FlipFlop: Schematic

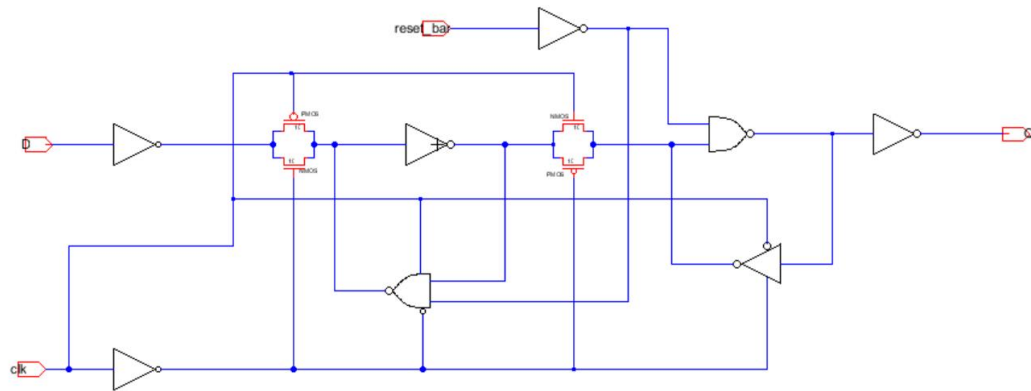

Layout

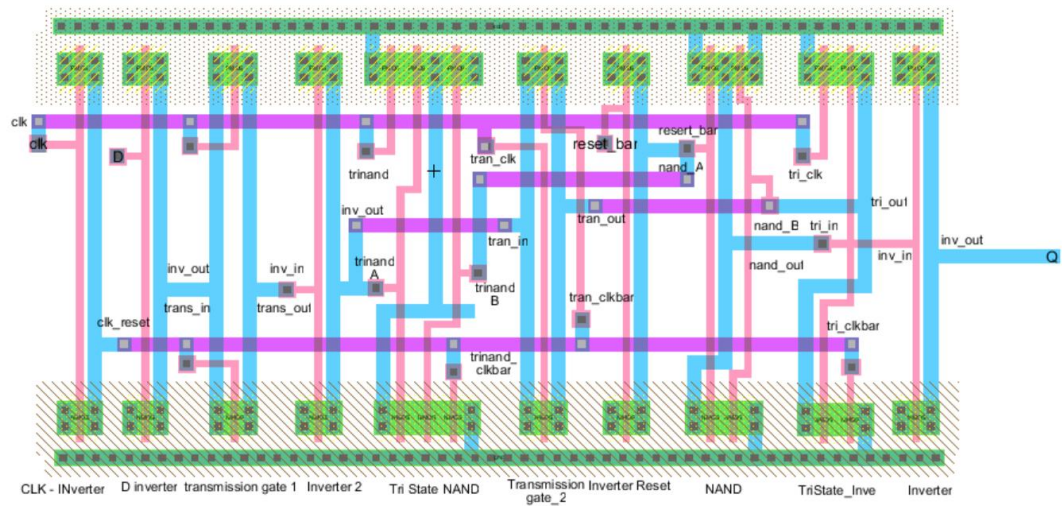

16-bit Accumulator Layout:

